

Problems

1. In a RC type generator, the maximum charging voltage is 80 V and the charging capacitor is 100 μF . Determine spark energy.
2. If in a RC type generator, to get an idle time of 500 μs for open circuit voltage of 100 V and maximum charging voltage of 70 V, determine charging resistance. Assume $C = 100 \mu\text{F}$.
3. For a RC type generator to get maximum power dissipation during charging $V_c^* = V_o \times 0.716$. Determine idle time for $R_c = 10 \Omega$ and $C = 200 \mu\text{F}$
4. Determine on time or discharge time if $V_o = 100 \text{ V}$ and $V_d^* = 15 \text{ V}$.
Spark energy = 0.5 J. Generator is expected for maximum power during charging.
Machine resistance = 0.5 Ω .

5. در یک مدار RC ژنراتور تولید جرقه برای ماشین EDM مقدار R مساوی 10 اهم و مقدار C مساوی 1 میکروفاراد است. اگر ولتاژ منبع 300 ولت باشد ماکزیمم توان جرقه چند وات خواهد بود؟